

Name: \_\_\_\_\_

ID#: \_\_\_\_\_

Section: \_\_\_\_\_

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO**

Problem	Weight	Score
1	25	
2	25	
3	25	
4	25	
Total	100	

### Test Form A

This test consists of four problems. Answer each problem on the exam itself; if you use additional paper, repeat the identifying information above, and staple it to the rest of your exam when you hand it in.

Problem 1: (25 Points)

1. (10 points) Consider the signal  $f(t)$  shown in Figure 1. Sketch the signals

$$g(t) = f(-2t)$$

and

$$h(t) = f(3 - 2t)$$

using the graphs provided in Figure 2.

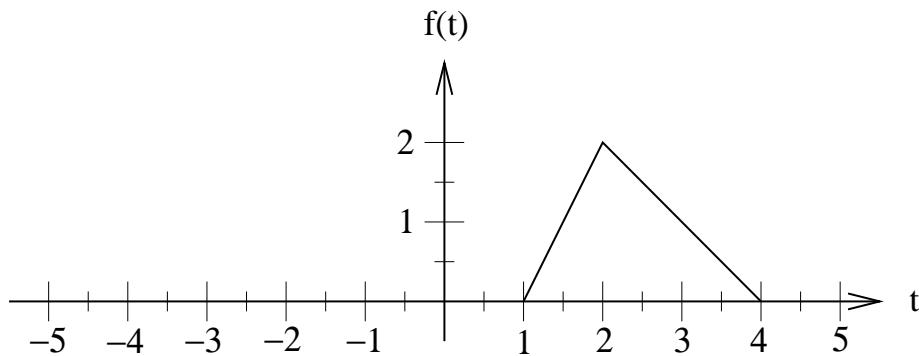


Figure 1: The signal  $f(t)$ .

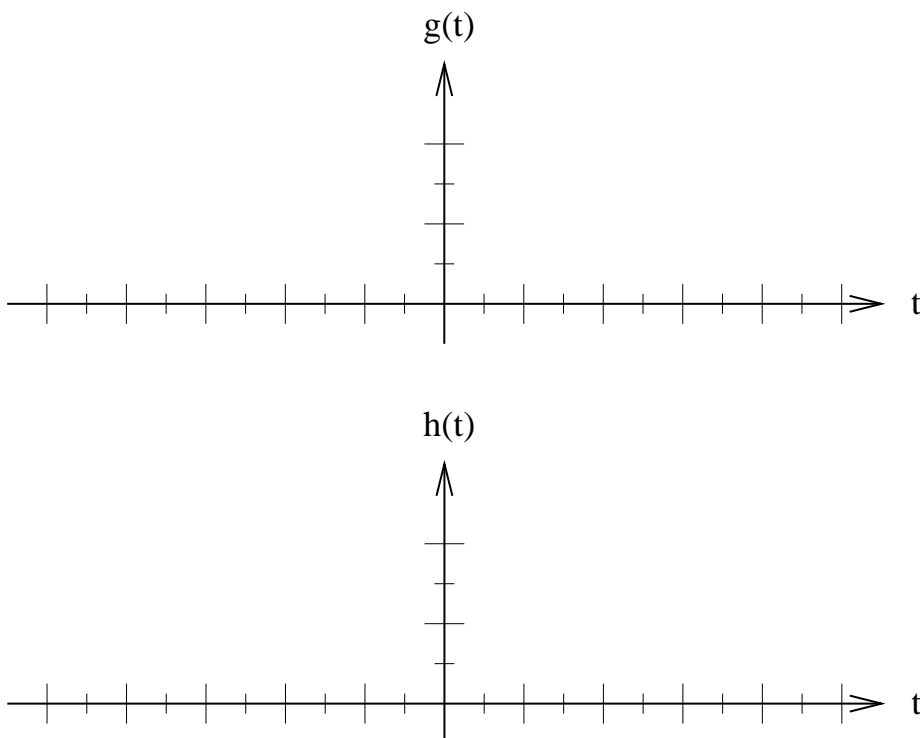


Figure 2: Blank graphs for sketching  $g(t)$  and  $h(t)$ .

2. (5 Points) Express the function

$$f(t) = e^{-t} u(t)$$

as the sum of an even function  $f_e(t)$  and an odd function  $f_o(t)$ .

3. (10 Points) The circuit shown in Figure 3 is driven by an independent voltage source with amplitude

$$f(t) = 8e^{-2t} u(t) \text{ V.}$$

Determine the energy (in Joules) that is dissipated as heat in the resistor  $R_1$  over the time interval

$$0 \leq t \leq \frac{\ln(2)}{4} \text{ s.}$$

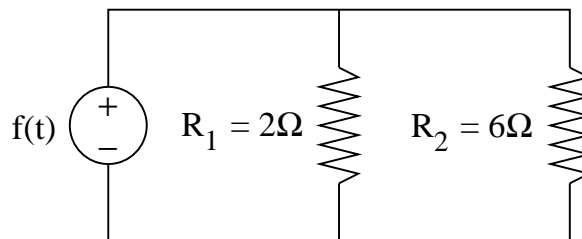


Figure 3: Resistive circuit with independent voltage source  $f(t)$ .

Problem 2: (25 points)

- (10 points) When applied to a linear time-invariant (LTI) system, the input  $f(t)$  shown in Figure 4(a) results in a zero-state response  $y(t)$ . A new input  $f_1(t)$  shown in Figure 4(b) is applied to the same LTI system. Express the resulting zero-state response  $y_1(t)$  in terms of  $y(t)$ .

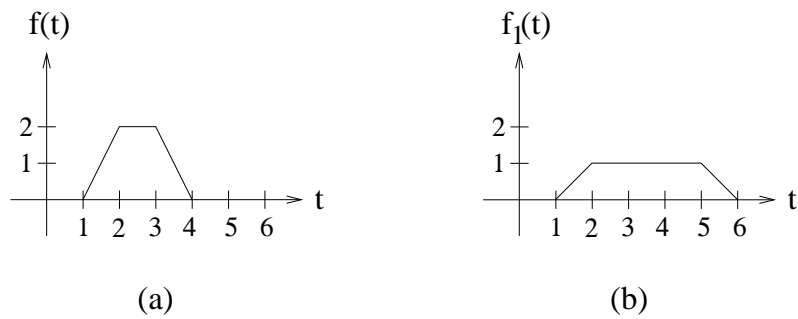


Figure 4: Inputs  $f(t)$  and  $f_1(t)$ .

2. (6 points) Give an example of a system that is both dynamic and noncausal. Write the mathematical description of the system and indicate why it is dynamic and noncausal.

3. (9 points) A second order LTI system with input  $f(t)$  and output  $y(t)$  is specified by the ODE

$$\frac{d^2 y}{dt^2} + 2 \frac{dy}{dt} - 8 y(t) = 10 f(t).$$

Determine whether the system is asymptotically stable or unstable.

Problem 3: (25 points)

The circuit shown in Figure 5 with input  $f(t)$  and output  $y(t)$  is described by the ODE

$$\frac{dy}{dt} + 3000 y(t) = \frac{1}{4} \frac{df}{dt}.$$

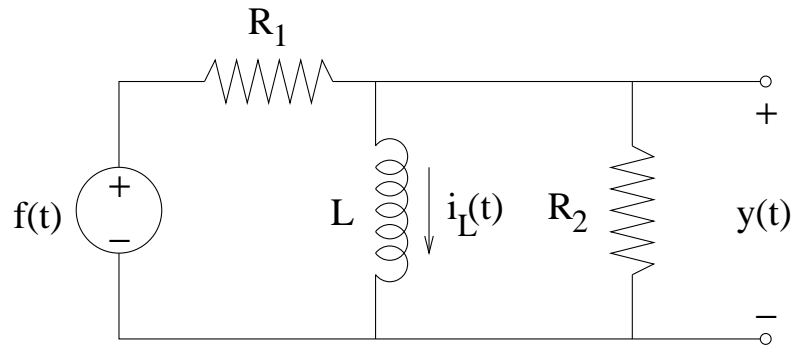


Figure 5: Circuit with input  $f(t)$  and output  $y(t)$ .

1. (8 points) Assume that  $R_1 = 300 \Omega$ ,  $R_2 = 100 \Omega$ ,  $L = 25 \text{ mH}$ , and the initial inductor current  $i_L(0)$  is 40 mA. Find the zero-input response of the circuit for  $t \geq 0$ .


2. (3 points) When a system is strictly proper, that is, when the order  $n$  of  $Q(D)$  is greater than the order  $m$  of  $P(D)$ , the zero-state response  $y_{zs}(t)$  at time  $t = 0$  must be zero. However, for proper ( $m = n$ ) or improper ( $m > n$ ) systems it is possible that  $y_{zs}(0) \neq 0$ . For the circuit shown in Figure 5 (redrawn below, where  $R_1 = 300 \Omega$ ,  $R_2 = 100 \Omega$ ,  $L = 25 \text{ mH}$ ) the ODE

$$\frac{dy}{dt} + 3000 y(t) = \frac{1}{4} \frac{df}{dt}$$

is proper because  $m = n = 1$ . Find the value of the zero-state response  $y_{zs}(t)$  at  $t = 0$  ( $y_{zs}(0) \neq 0$ !) assuming that  $i_L(0) = 0 \text{ A}$  (no stored energy at time  $t = 0$ ) and

$$f(t) = 4 e^{-1000 t}$$

for  $t \geq 0$ .

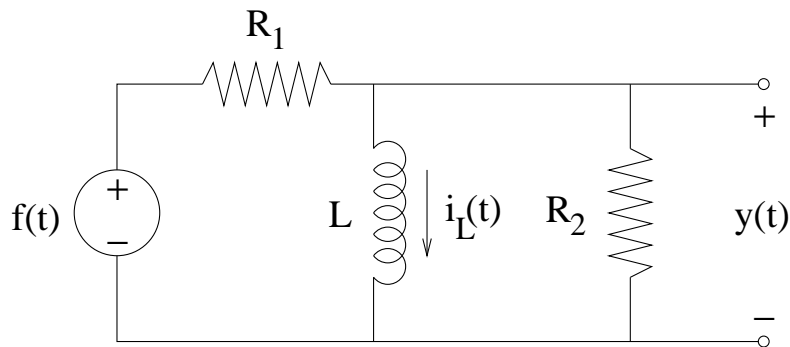

3. (5 points) Using the value of  $y_{zs}(0)$  calculated in part (2) and the input

$$f(t) = 4 e^{-1000 t}$$

for  $t \geq 0$ , find the zero-state response  $y_{zs}(t)$  of the circuit shown above for  $t \geq 0$ .





4. (9 points) Now consider an RC circuit with input  $f(t)$  and output  $y(t)$  that is described by the differential equation

$$\frac{dy}{dt} + \frac{1}{RC} y(t) = \frac{1}{RC} f(t).$$

Given that  $C = 0.1 \mu\text{F}$ , determine the value of  $R$  so that the response of the circuit to a unit step input has a 10% to 90% rise-time of  $\ln(9)$  ms.

Problem 4: (25 points)

The switch in Figure 6 has been closed long enough for the voltages and currents to reach steady-state values. At time  $t = 0$  the switch is opened. Assume that  $V_1 = 2$  V,  $V_2 = 4$  V,  $L = 50$  H,  $C = 1250$   $\mu$ F, and  $R = 40$   $\Omega$ .

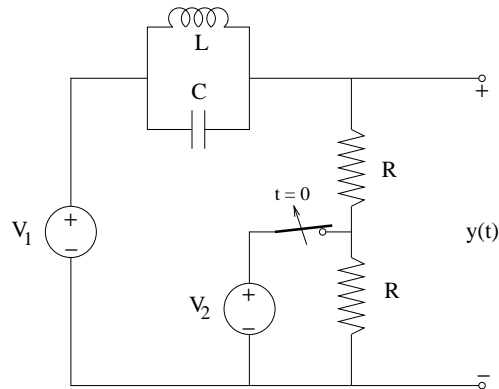


Figure 6: The switch has been closed a very long time before it is opened at time  $t = 0$ .

- (6 points) Find the initial conditions

$$y(0^+) = \text{---} \text{ V}$$

$$\left. \frac{dy}{dt} \right|_{t=0^+} = \text{---} \frac{\text{V}}{\text{s}}$$

2. (6 points) Once again consider the circuit shown in Figure 6 (redrawn below) where the switch is opened at  $t = 0$  and  $V_1 = 2 \text{ V}$ ,  $V_2 = 4 \text{ V}$ ,  $L = 50 \text{ H}$ ,  $C = 1250 \mu\text{F}$ , and  $R = 40 \Omega$ . Find a second-order ODE of the form

$$\frac{d^2 y}{dt^2} + \underline{\hspace{1cm}} \frac{dy}{dt} + \underline{\hspace{1cm}} y(t) = \underline{\hspace{1cm}}$$

that describes the behavior of  $y(t)$  for  $t \geq 0$ .

